

DATE

SHEET NO.

GROUP NO: 44

NAME: AVIJIT MANDAL (18CS30010)
SUMIT KUMAR YADAV (18CS30042)

DATE

SHEET NO.

AIM OF EXPERIMENT (Part 2) :-

Design a 3-bit to 8-bit encoder using NAND and NOR gates, having the following input/output behaviour.

x	y	z	a	b	c	d	e	f	g	h
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	1
0	1	0	0	0	0	0	0	1	1	1
0	1	1	0	0	0	0	0	1	1	1
1	0	0	0	0	0	1	1	1	1	1
1	0	1	0	0	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1

APPARATUS REQUIRED:

- (i) 74LS00 x 3
- (ii) 74LS02 x 1

Theory :-

NAND and NOR are universal gates, that is any boolean function can be realized by using only NAND gates or only NOR gates. We have:

$$x' = (1 \cdot x)' \quad [\text{NOT}]$$

$$xy = ((xy)')' = (1 \cdot (xy)')' \quad [\text{AND}]$$

$$x+y = (x'y')' = ((1 \cdot x)' (1 \cdot y)')' \quad [\text{NOR}]$$

This means that the three basic boolean operations AND, OR and NOT can be realized by NAND gates.

for NOR gates, we have dual formulas:-


$$x' = (0 + x)' \quad [\text{NOT}]$$

$$x+y = ((x+y)')' = (0 + (x+y)')' \quad [\text{OR}]$$

$$xy = (x'+y')' = ((0+x)' + (0+y)')'$$

Circuit Diagram :-

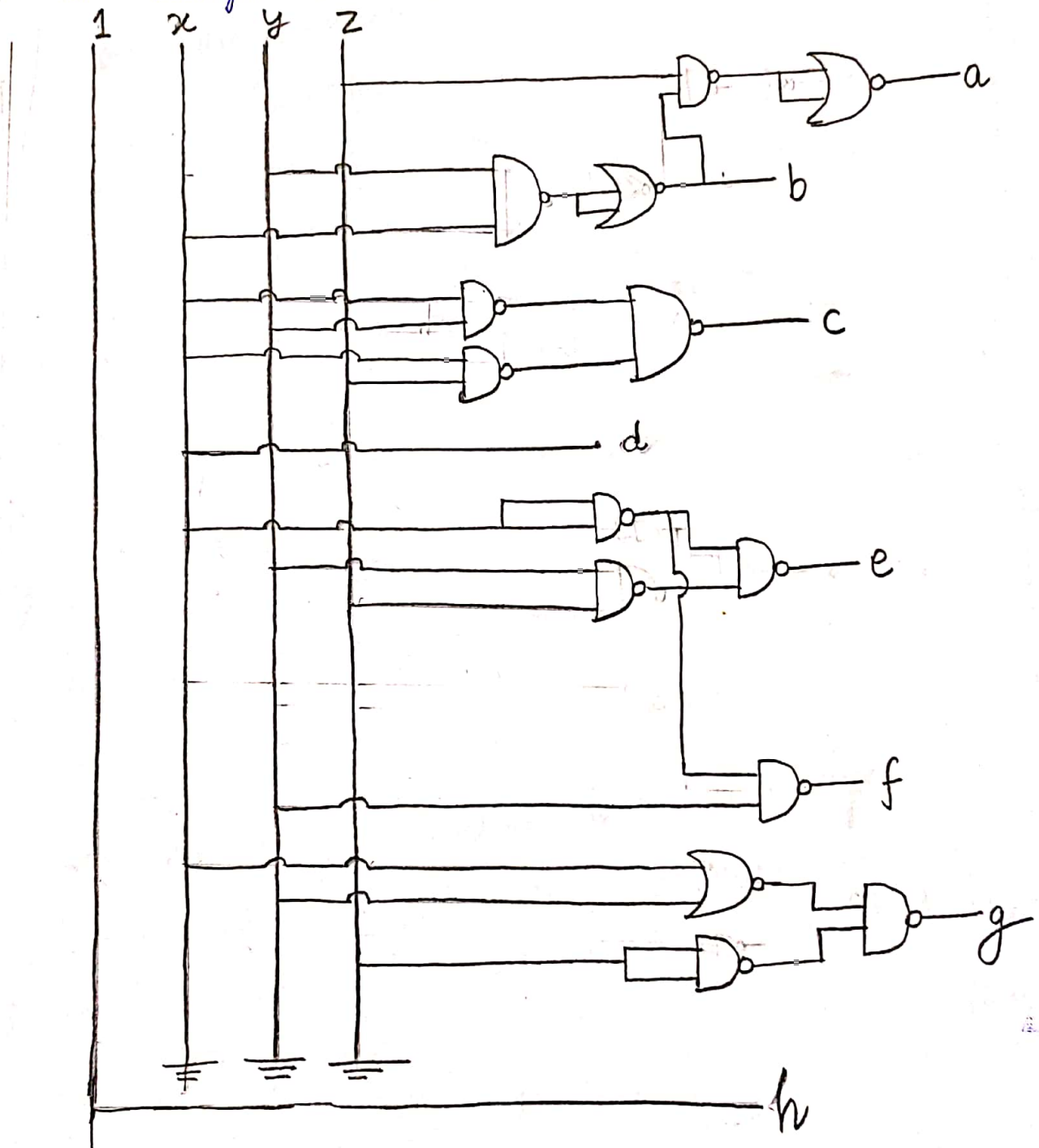We used the following combinational logic circuit to design the 3-bit to 8-bit encoder :-



OBSERVATIONS

We observed the following are switching functions for the output

Implementation

$$a = xyz \longrightarrow \overline{\overline{xy} \cdot \overline{z}} = xyz$$

$$b = xy \longrightarrow \overline{\overline{x} \cdot \overline{y}} = xy$$

$$c = xy + xz \longrightarrow \overline{\overline{x \cdot z} + \overline{xy}} = xz + xy$$

$$d = x \longrightarrow x$$

$$e = x + yz \longrightarrow \overline{\overline{yz} \cdot \overline{x}} = x + yz$$

$$f = x + y \longrightarrow \overline{\overline{x} \cdot \overline{y}} = x + y$$

$$g = x + y + z \longrightarrow \overline{\overline{x+y} \cdot \overline{z}} = x + y + z$$

$$h = 1 \longrightarrow 1$$

For above switching functions, and the circuit diagram, when input x, y, z were provided, we got the desired outputs. when red light showed, it implied high (1) and Green light showed, it implied low (0).

Result:-

The following switching functions correctly produce the desired output :-

$$a = xyz$$

$$e = x + yz$$

$$b = xy$$

$$f = x + y$$

$$c = xy + xz$$

$$g = x + y + z$$

$$d = x$$

$$h = 1$$

- The above implementation required 12 NAND gates and 4 NOR gates. Thus, we required 74LS00 (number = 3) and 74LS02 (number = 1) to successfully implement the 3-bit to 8-bit encoder.