

PART : 2
(Circuits for Error Correction Codes (ECC))

Aim:


Design, implementation and testing for:

1. Module -1:BCD to BCD ECC for single-bit error
2. Module -2:Recovery of BCD form BCD ECC with error of up to 1-bit
3. Module -1:should take input through a thumbwheel (may have to be shared with other group) or directly from terminals on the kit (if thumbwheel is not available)
4. The output of module -1 should be the input to moduie -2 with XOR gates in between to artificially inject errors
5. The output of module -2 should be connected to the 7- segment display for BCD designed in the previous part.

Apparatus Required:

 1. IC 4030 *6
2. 4*16 Decoder

Circuit Diagram for Module-1: BCD to BCD ECC for single bit error (Hamming code)



Design:

Module-1:

B1	B2	B3	B4	P1	P2	B1	P3	B2	B3	B4
0	0	0	0	1	1	0	1	0	0	0
0	0	0	1	0	0	0	0	0	0	1
0	0	1	0	1	0	0	0	0	1	0
0	0	1	1	0	1	0	1	0	1	1
0	1	0	0	0	1	0	0	1	0	0
0	1	0	1	1	0	0	1	1	0	1
0	1	1	0	0	0	0	1	1	1	0
0	1	1	1	1	1	0	0	1	1	1
1	0	0	0	0	0	1	1	0	0	0
1	0	0	1	0	1	1	0	0	0	1

Module-2:

Ci - Boolean value is '1' if the priority condition involving bit Pi is violated.

$$C1 = P1 \oplus b1 \oplus b2 \oplus b4$$

$$C2 = P2 \oplus b1 \oplus b3 \oplus b4$$

$$C3 = P3 \oplus b2 \oplus b3 \oplus b4$$

fi (error flag) - Boolean value is '1' if error has occurred in bit Pi

$$\Rightarrow f1 = e1.e2'.e3'$$

$$f2 = e1'.e2.e3'$$

$$f3 = e1'.e2'.e3$$

gi(error flag) - Boolean value is '1' if error has occurred in bit bi

$$\Rightarrow g1 = e1.e2.e3'$$

$$g2 = e1.e2'.e3$$

$$g3 = e1'.e2.e3$$

$$g4 = e1.e2.e3$$

Recomputing received bits to the correct bits: b-received bit, br : recovered correct bit

$$\Rightarrow Pr1 = P1 \oplus f1$$

$$Pr2 = P2 \oplus f2$$

$$Pr3 = P3 \oplus f3$$

$$br1 = b1 \oplus g1$$


$$br2 = b2 \oplus g2$$

$$br3 = b3 \oplus g3$$

$$br4 = b4 \oplus g4$$

- We force an error in Hamming code generated in module-1 by using XOR gate: passing a bit through XOR gate and giving it as input to module-2 along with six other outputs of module-1.

 Circuit Diagram for Module-2: Recovery of BCD from BCD ECC with error of up to 1-bit



Circuit Diagram for Module: Output of module-1 should be the input to module-2 with XOR gates in between to artificially inject errors

