

**PART : 3**  
**( Fault-Tolerant Signal Display )**

**Aim:**

Two signals are to be present, green and red (as LEDs). These are to be driven by transistors circuits. Bit g is to drive the green signal and g' is to drive the red signal. If the green LED fails (becomes an open circuit), the red LED should be lit, instead (even though g=1).

**Apparatus Required:**

1. BC541 \*2
2. 74LS500 \*1
3. Green LED
4. Red LED
5. Resistors (4.7K ohm) \*2

**Theory:**


1. LEDs are driven by transistors circuits.
2. LED is connected to the emitter region of the NPN transistor(BC541).
3. +5V is given the collector region of the NPN transistor.
4. LED glows whenever we give input at the base.
5. As the potential is applied at the base, it makes emitter-base junction in forward bias and base-collector in reverse bias, active region, and current-flows, that results in the glow of LED.

**Design:**

Logic	RED	GREEN
0	1	0
1	0	1
Open Circuit	1	0

- a. Whenever '0' or NO input is given Red light glows.
- b. Whenever logic '1' is given Green light glows.

### Circuit Diagram:

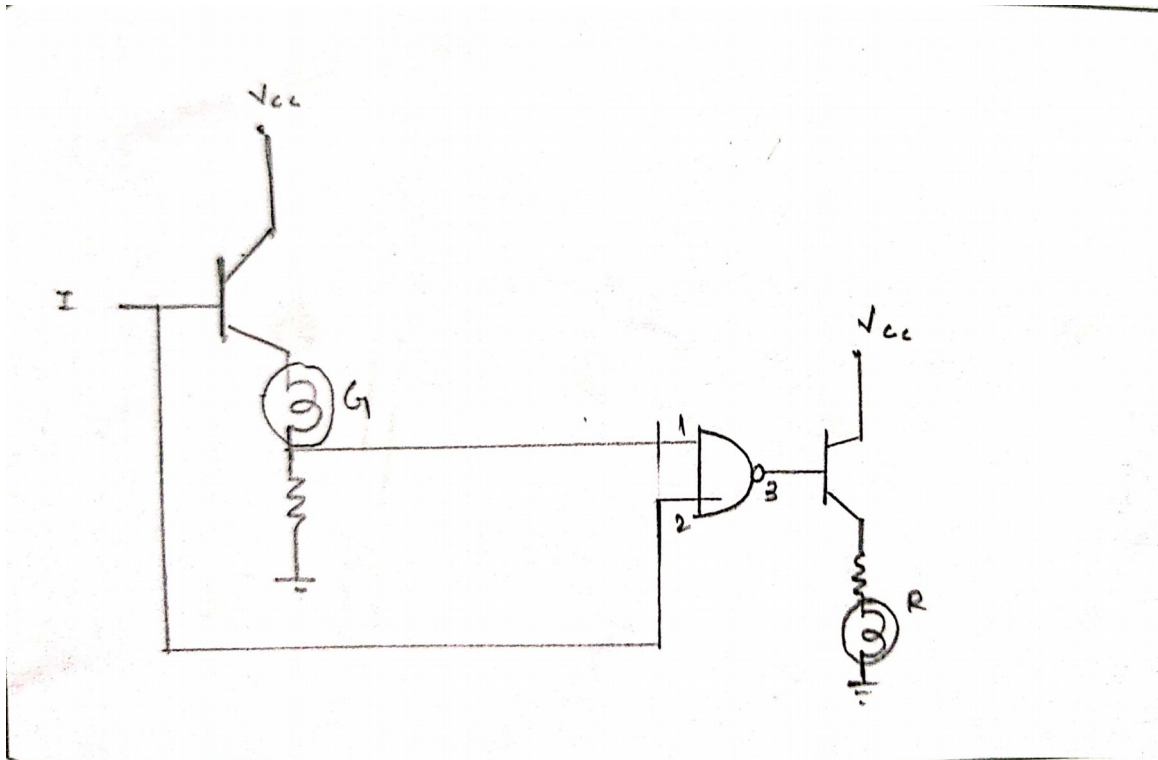

### Result:

The results are the same as explained.

### Discussion:

a. When the input g is supplied with high input signal, then the LED shows green i.e, green LED glows and the red LED is off and vice versa.